


# Half Adder



Equation for Sum & Carry:

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB = A \& B$$

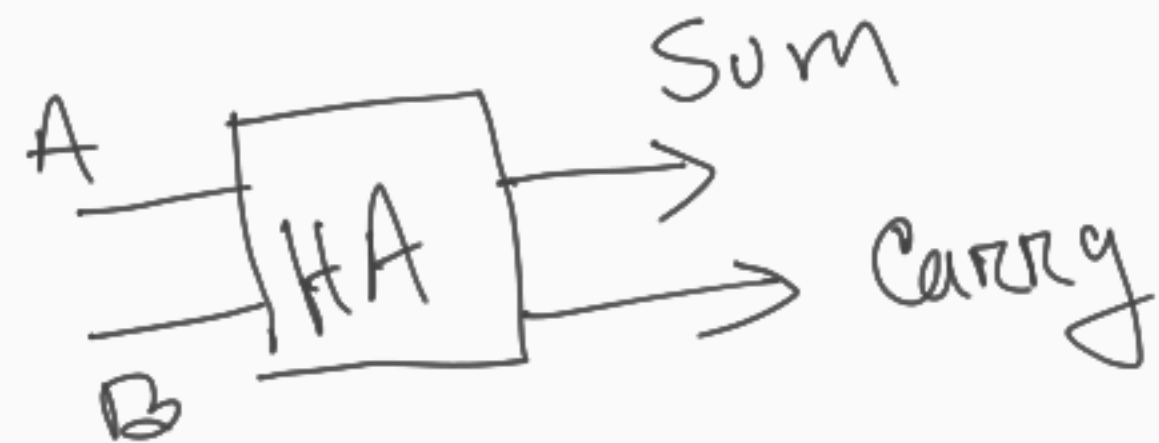

Truth table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Sketch for HA:

```
byte A, B;  
  
void setup() {  
  pinMode(13, OUTPUT);  
  pinMode(12, OUTPUT);  
  pinMode(11, INPUT);  
  pinMode(10, INPUT);  
}
```

```
void loop()  
{  
  A = digitalRead(11);  
  B = digitalRead(10);  
  
  digitalWrite(13, A & B);  
  digitalWrite(12, A & B);  
}
```

Suppose, 5 is the input you have to take the last two bits of this Number and show the half adder operation.

5  $\rightarrow$ 

8	4	2	1
0	1	0	1

A    B

$0 + 4 + 0 + 1 = 5$



# Full Adder

Truth table:

A	B	C	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



Equation:

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

Through k-Map:

	$\bar{A}\bar{B}$	$\bar{A}B$	$AB$	$A\bar{B}$
C	<del>0</del> 0	<del>1</del> 1	<del>3</del> 0	<del>2</del> 1
C	<del>4</del> 1	<del>5</del> 0	<del>7</del> 1	<del>6</del> 0

$$S = A \oplus B \oplus C$$

Carry out:

	$\bar{A}\bar{B}$	$\bar{A}B$	$AB$	$A\bar{B}$
c	0	0	1	0
c	0	1	1	1

$$C = AB + BC + AC$$

Sketch for FA:

OR  $\rightarrow$  1

```
byte A, B, C;  
void setup() {  
  pinMode(13, OUTPUT);  
  pinMode(12, OUTPUT);  
  pinMode(7, INPUT);  
  pinMode(8, INPUT);  
  pinMode(9, INPUT);  
}
```

```
void loop() {  
  A = digitalWrite(7);  
  B = digitalWrite(8);  
  C = digitalWrite(9);  
  digitalWrite(12, A & B & C);  
  digitalWrite(13, (A & B) |  
    (B & C) | (A & C));  
}
```

Suppose, 6 is the number you have. Now, you have to take the last 3 bits of this number as input and show the Full adder operation

→ 6 = 

1	0	1	1	0
---	---	---	---	---





